

Logic Design Final Lab

Designing a Microprocessor

2024-13755 | 김연준

Class 3, Team 12

Dept. of Computer Science and Engineering

Submission files

1	LDLAB_250617_class003_team12_김연준_2024-13755.pdf	Final Lab report file
2	Proc.v	Code
3	proctest.v	Testbench Code
4	Alu.v	Code
5	DMem.v	Code
6	freqDivider.v	Code
7	HexTo7Seg.v	Code
8	Imem.v	Code
9	Opcode2Seg.v	Code
10	RegFile.v	Code
11	RegWriteTo7Seg.v	Code
12	Proc.ucf	User constraint file

1. Overall Design and Structure

The main module of our microprocessor is implemented in `Proc.v`.

```
module Proc(  
    input [7:0] inst,  
    output [7:0] readAddr,  
    output [6:0] segOut16,  
    output [6:0] segOut1,  
    output [6:0] segPc16,  
    output [6:0] segPc1,  
    output [6:0] segOpcode,  
    output negLED,  
    input CLK_osc,  
    input RST,  
    input HALT  
);
```

The input and output are as shown above. It receives the oscillator's clock, and instruction as input, and outputs 7 segment signals for instruction result. There are also additional ports for my team's additional features.

1.1. Frequency divider

```
31 // *** Clock (Frequency Divider) ***  
32 wire CLK;  
33 wire haltCLK; // for additional feature  
34 freqDivider fDiv (  
35     .clr(RST),  
36     .HALT(HALT),  
37     .CLK(CLK_osc),  
38     .CLKout(CLK),  
39     .haltCLKout(haltCLK)  
40 );  
41
```

```
1 `timescale 1ns / 1ps  
2  
3 module freqDivider(  
4     input clr,  
5     input HALT,  
6     input CLK,  
7     output reg CLKout,  
8     output reg haltCLKout  
9 );  
10  
11 reg[31:0] cnt;  
12 reg[31:0] haltCnt;  
13  
14 always @(posedge CLK) begin  
15     if (clr) begin  
16         cnt <= 32'd0;  
17         haltCnt <= 32'd0;  
18  
19         CLKout <= 1'b1;  
20         haltCLKout <= 1'b1;  
21     end  
22     else if (HALT == 0) begin // ordinary clock  
23         if (cnt == 32'd0) begin // for simulation test  
24             //if (cnt >= 32'd25000000) begin  
25                 cnt <= 32'd0;  
26                 CLKout <= ~CLKout;  
27             end  
28         else begin  
29             cnt <= cnt + 1;  
30         end  
31     end  
end
```

We implemented the frequency divider in `freqDivider.v`. It converts a 50MHz oscillator input into a 1Hz clock signal. 'haltCLK' is something for one of our additional features. (see section 3 for details)

1.2. Decoding instructions and assigning control signals

```
67     assign iOpcode = inst[7:6];
68     assign iRs = inst[5:4];
69     assign iRt = inst[3:2];
70     assign iRd = inst[1:0];
71     assign iImm = {{6{inst[1]}}, inst[1:0]}; // imm = signExtend(inst[1:0])
72
73     // (2) Control Signals
74     wire [7:0] control;
75     wire cRegDst;
76     wire cRegWrite;
77     wire cALUSrc;
78     wire cBranch;
79     wire cMemRead;
80     wire cMemWrite;
81     wire cMemtoReg;
82     wire cALUOp;
83     assign {cRegDst, cRegWrite, cALUSrc, cBranch,
84             cMemRead, cMemWrite, cMemtoReg, cALUOp} = control;
85     assign control =
86         (iOpcode == 2'b00) ? 8'b11000001 : // add
87         (iOpcode == 2'b01) ? 8'b01101010 : // lw
88         (iOpcode == 2'b10) ? 8'b00100100 : // sw
89         (iOpcode == 2'b11) ? 8'b00010000 : 0; // j
```

This part of `Proc.v` decodes the instruction input into multiple variables and assigns control signals (variables with 'c' prefixes) according to the opcode.

1.3. The register file

```
91     // (3) Register File
92     wire [7:0] read1;
93     wire [7:0] read2;
94     wire [1:0] wIdx;
95     wire [7:0] wData;
96
97     // * Additional Feature *
98     //Connecting MSB of wData to negLED, c
99     assign negLED = wData[7];
100
101     RegFile rFile(
102         .rIdx1(iRs),
103         .rIdx2(iRt),
104         .write(cRegWrite),
105         .wIdx(wIdx),
106         .wData(wData),
107         .read1(read1),
108         .read2(read2),
109         .CLK(CLK),
110         .RST(RST)
111     );
112
```

```
1  `timescale 1ns / 1ps
2
3  module RegFile(
4      input [1:0] rIdx1,
5      input [1:0] rIdx2,
6      input write, // write enable
7      input [1:0] wIdx,
8      input [7:0] wData,
9      output [7:0] read1,
10     output [7:0] read2,
11     input CLK,
12     input RST
13 );
14
15     reg [7:0] regFile [3:0];
16
17     assign read1 = regFile[rIdx1];
18     assign read2 = regFile[rIdx2];
19
20     // Initialize Register File
21     always @ (posedge CLK or posedge RST) begin
22         if(RST == 1) begin
23             regFile[0] = 8'b0;
24             regFile[1] = 8'b0;
25             regFile[2] = 8'b0;
26             regFile[3] = 8'b0;
27         end
28         else begin
29             if(write) begin
30                 $display("wData = %d, wIdx = %d", wData, wIdx);
31                 regFile[wIdx] = wData;
32             end
33         end
34     end
35 endmodule
```

The register file module is defined at `RegFile.v`. The `RegFile` module has 4 data registers. The module is synchronized to the processor clock and handles data write and read.

1.4. The ALU

```
1  `timescale 1ns / 1ps
2
3  module Alu(
4      input [7:0] val1,
5      input [7:0] val2,
6      input aluOp,
7      output [7:0] result
8  );
9
10     wire [7:0] res;
11     wire [7:0] v1, v2;
12
13     assign v1 = val1;
14     assign v2 = val2;
15     assign result = res;
16
17     assign res = v1 + v2;
18
19     always@(res) begin
20         // $display("%d+ %d = %d", v1, v2, res);
21     end
22 endmodule
23
```

The part of `Proc.v` at the top and `Alu.v` at the bottom implements the ALU. ALU is a purely combinational module and was implemented with data flow style description.

1.5. The Data Memory

```
130 // (5) Data Memory
131 wire [7:0] memAddr;
132 wire [7:0] memWData;
133 wire [7:0] memRData;
134
135 assign memWData = read2;
136 assign memAddr = aluOut;
137
138 DMem dMem(
139     .Address(memAddr),
140     .writeData(memWData),
141     .readData(memRData),
142     .MemRead(cMemRead),
143     .MemWrite(cMemWrite),
144     .CLK(CLK),
145     .RST(RST)
146 );
```

```
1  `timescale 1ns / 1ps
2
3  module DMem(
4      input [7:0] Address,
5      input [7:0] writeData,
6      output [7:0] readData,
7      input MemRead,
8      input MemWrite,
9      input CLK,
10     input RST
11 );
12
13     reg [7:0] mem [0:31];
14     wire [7:0] wD;
15     wire [7:0] rD;
16     wire [7:0] addr;
17
18     assign addr = Address;
19     assign wD = writeData;
20     assign readData = rD;
21
22     assign rD = (MemRead==1) ? mem[addr] : 0;
23
24     integer i = 0;
25     always @(posedge CLK or posedge RST) begin
26         if (RST == 1) begin
27             for(i = 0; i < 16; i = i+1) begin
28                 mem[i] = i;
29                 mem[16+i] = -i;
30                 // $display("%d", mem[16+i]);
31             end
32         end
33         else begin
34             if (MemWrite == 1) begin
35                 $display("wData: %d", wD);
36                 mem[addr] = wD;
37             end
38         end
39     end
40
41 endmodule
42
43
```

The part of `Proc.v` at the top and `DMem.v` at the bottom implements the data memory. This part manages the reading/writing of data to the data memory. The `DMem` module is synchronized to the processor's clock.

1.6. Writing back to register file and output

```

148 // (6-1) Write Back
149 assign wIdx = (cMemtoReg == 0) ?
150     iRd : // (op == add) rd
151     iRt; // (op == lw) rt
152 assign wData =
153     (iOpcode == 2'b00) ? aluOut : // (op == add) rs+rt
154     (iOpcode == 2'b01) ? memRData : // (op == lw) Mem[rs+imm]
155     8'b0; // (op == sw) or (op == j)
156
157
158 // (6-2) 7Seg output converter
159 RegWriteTo7Seg to7segOut (
160     .reg_data(wData),
161     .seg_high(sOut16),
162     .seg_low(sOut1)
163 );
164

```

The part of `Proc.v` shown above controls the register write index and data signals according to opcode and operation results. Also, the write data (`wData`) is displayed at two 7-segment cells. In the final lab announcement pdf file, it was not specified what we should display for 'sw' and 'j' instruction results. So, our processor just always displays '00' for 'sw' and 'j' instructions.

```

21 module RegWriteTo7Seg(
22     input [7:0] reg_data,
23     output [6:0] seg_high,
24     output [6:0] seg_low
25 );
26
27 wire [3:0] high = reg_data[7:4];
28 wire [3:0] low = reg_data[3:0];
29
30 HexTo7Seg high_display (
31     .hex(high),
32     .seg(seg_high)
33 );
34
35 HexTo7Seg low_display (
36     .hex(low),
37     .seg(seg_low)
38 );
39
40 endmodule
41

```

```

21 module HexTo7Seg(
22     input [3:0] hex, // 4-bit hex input
23     output reg [6:0] seg // 7-seg output (a~g)
24 );
25
26 always @(*) begin
27     case(hex)
28         4'h0: seg = 7'b111_1110; // abc_defg
29         4'h1: seg = 7'b011_0000;
30         4'h2: seg = 7'b110_1101;
31         4'h3: seg = 7'b111_1001;
32
33         4'h4: seg = 7'b011_0011;
34         4'h5: seg = 7'b101_1011;
35         4'h6: seg = 7'b101_1111;
36         4'h7: seg = 7'b111_0000;
37
38         4'h8: seg = 7'b111_1111;
39         4'h9: seg = 7'b111_1011;
40         4'hA: seg = 7'b111_0111;
41         4'hB: seg = 7'b001_1111;
42
43         4'hC: seg = 7'b100_1110;
44         4'hD: seg = 7'b011_1101;
45         4'hE: seg = 7'b100_1111;
46         4'hF: seg = 7'b100_0111;
47         default: seg = 7'b000_0000; // all segments off
48     endcase
49 end
50
51 endmodule
52

```

The conversion to binary data to hexadecimal 7-segment output is performed by the 'RegWriteTo7Seg' module. It is defined at `RegWriteTo7Seg.v` as shown above. it comprises two submodules 'HexTo7Seg', which is defined at `HexTo7Seg.v`.

1.7. Handling RST input and Updating PC

```
179 // *** Behavior ***
180
181 always @(posedge CLK or posedge RST) begin
182     if(RST == 1) begin
183         // Initialize / Reset processor
184         pc <= 8'b0;
185     end
186     else begin
187         // Update PC
188         $display("pc: %d", pc);
189         pc <= (cBranch==0) ?
190             (pc+1) : // (op != j)
191             (pc+1 + iImm); // (op == j)
192     end
193 end
194
195 endmodule
```

The part of `Proc.v` shown above describes the synchronous behavior of our processor. The next PC is determined regarding whether the instruction is 'j' or not. The RST (Reset) signal is given asynchronously and resets the processor immediately. The synchronous submodules of Proc (RegFile and DMem) also share the RST signal, and they are also reset as the signal is given.


2. Simulation and FPGA Implementation Results

2.1. Simulation results

```
21 module imem(
22     output [7:0] instruction,
23     input [7:0] Read_Address
24 );
25
26 wire [7:0] MemByte[31:0];
27
28 // *** test program 1 ***
29
30 assign MemByte[0] = 8'b01001001;
31 assign MemByte[1] = 8'b11000001;
32 assign MemByte[2] = 8'b00011000;
33 assign MemByte[3] = 8'b10101001;
34 assign MemByte[4] = 8'b01001101;
35
36
37
38
39
40
41
42
43
44
45
46
47
48
49
50
51
52
53
54
55
56
57
58
59
60
61
62
63
64
65
66
67
68
69
70 assign instruction = MemByte[Read_Address];
71
72 endmodule
73
```

We tested out design with some programs we made according to the ISA. (The pseudocodes, machine codes, and the expected output of our testing programs are documented at **Appendix**.) The instruction memory module defined at `imem.v` shown above, replaces the role of the TA board used for actual testing. In all three programs we wrote, the output results (the values `segOut1` and `segOut16`) were as anticipated. The simulation results – both waveform and console outputs - are shown below.

Simulation result for program 1.


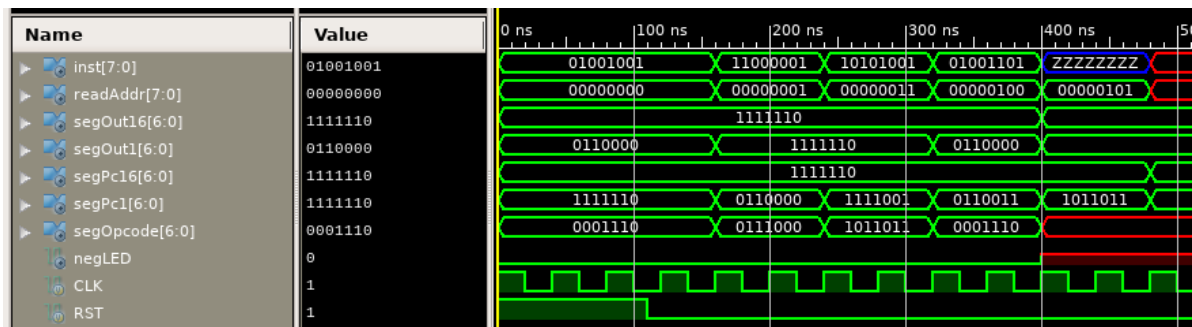


```

pc: 0
wData = 1, wIdx = 2
pc: 1
pc: 3
wData: 1
pc: 4
wData = 1, wIdx = 3
pc: 5
pc: x
pc: x

```



Simulation result for program 2.

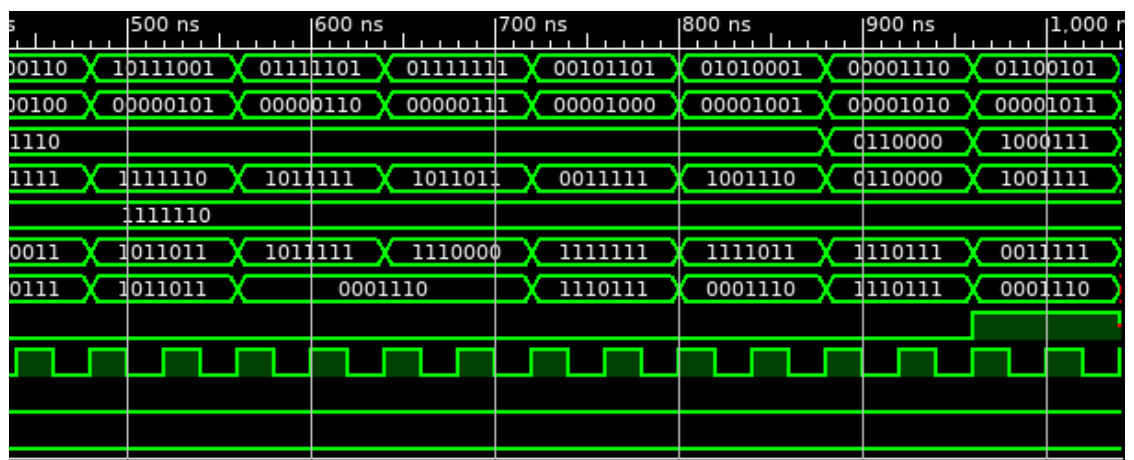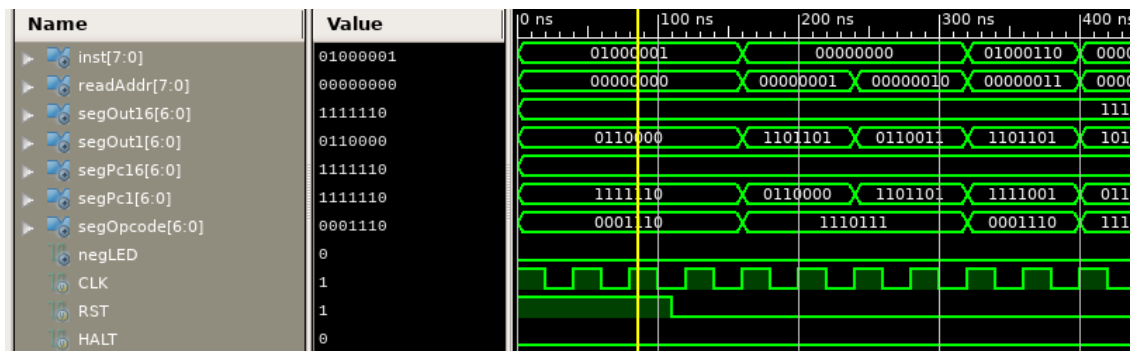

pc: 0 wData = 1, wIdx = 0 pc: 1 wData = 2, wIdx = 0 pc: 2 wData = 4, wIdx = 0 pc: 3 wData = 2, wIdx = 1 pc: 4 wData = 6, wIdx = 2 pc: 5 wData: 6 pc: 6 wData = 6, wIdx = 3	pc: 7 wData = 5, wIdx = 3 pc: 8 wData = 11, wIdx = 1 pc: 9 wData = 12, wIdx = 0 pc: 10 wData = 17, wIdx = 2 # run 1.00us pc: 11 wData = 254, wIdx = 1 pc: 12
---	---


Console Compilation Log

Simulation result for program 3.

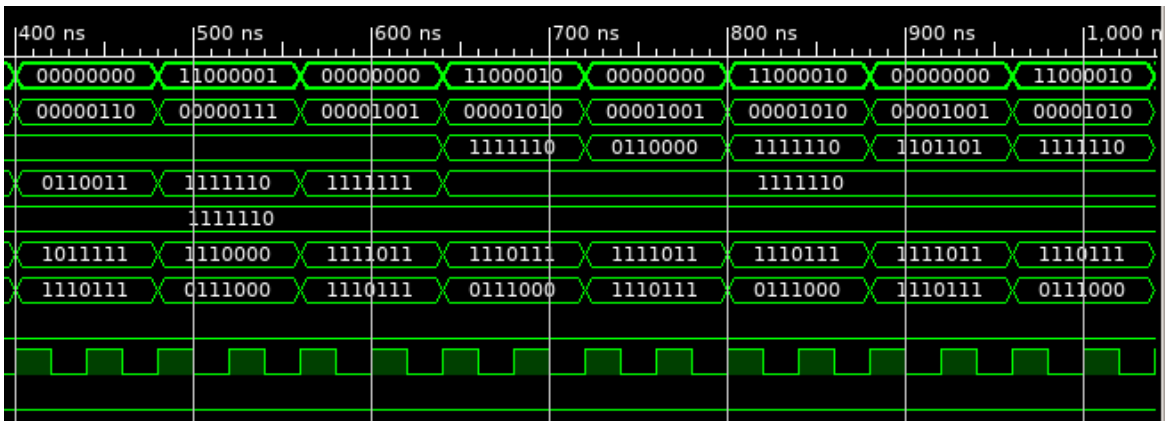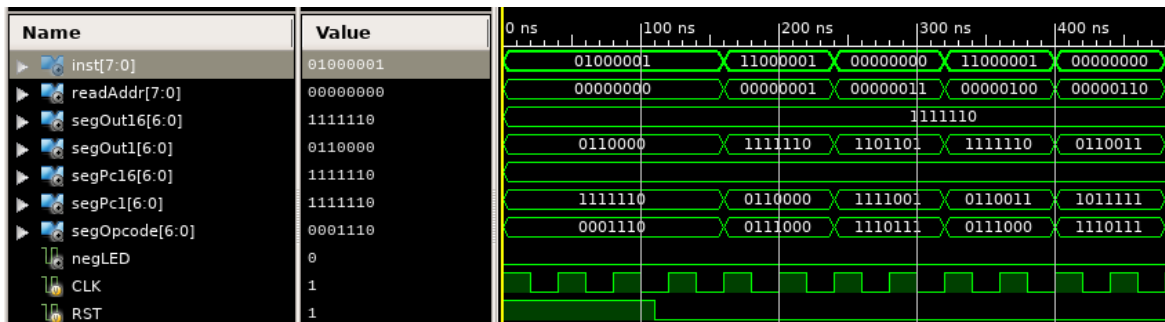

pc: 0 wData = 1, wIdx = 0 pc: 1 pc: 3 wData = 2, wIdx = 0 pc: 4 pc: 6 wData = 4, wIdx = 0 pc: 7 pc: 9 wData = 8, wIdx = 0	pc: 10 pc: 9 wData = 16, wIdx = 0 pc: 10 pc: 9 wData = 32, wIdx = 0 # run 1.00us pc: 10 pc: 9 wData = 64, wIdx = 0 pc: 10
---	---


2.2. FPGA implementation results

 

The figure above shows the FPGA implementation result of our microprocessor. The output values are displayed at the first and second 7-segment. Also, the sixth tactile switch is the reset button. The test results for FPGA implementation were consistent with our simulation results.

3. Additional Features

3.1. PC and Opcode display

 


```
165 // (6-3) *Additional Feature* display PC to 7seg
166 RegWriteTo7seg to7segPc (
167     .reg_data(pc),
168     .seg_high(sPc16),
169     .seg_low(sPc1)
170 );
171
172 // (6-3) *Additional Feature* output opcode to 7seg
173 Opcode2Seg opcode2seg (
174     .opcode(iopcode),
175     .seg(op2seg)
176 );
```

```
23 // *Additional Feature* display opcode to 7seg
24
25 module Opcode2Seg(
26     input [1:0] opcode,
27     output [6:0] seg
28 );
29
30 assign seg =
31     (opcode == 2'b00) ? 7'b1110111 : // 'A' (add)
32     (opcode == 2'b01) ? 7'b0001110 : // 'L' (lw)
33     (opcode == 2'b10) ? 7'b1011011 : // 'S' (sw)
34     (opcode == 2'b11) ? 7'b0111000 : 0; // 'J' (j)
35
36
37 endmodule
38
```

In addition to the output display, we put extra displays for the current PC and the opcode of current instruction. We showed the opcode as one of the symbolic characters (A, L, S, and J) through the Opcode2Seg module defined at Opcode2Seg.v. (Actually, this feature helped us debug the hardware).

3.2. Negative number output indicator

 


```
97 // * Additional Feature *
98 //Connecting MSB of wData to negLED, describing whether wData is negative.
99 assign negLED = wData[7];
100
```

We also added an LED display that indicates negative number outputs of an operation. The processor takes the MSB of the two's complement output and lights up the LED if the output is a negative number.

 3.3. Processor interrupt switch

We added a switch that interrupts the processor and halts the execution of instructions. But we thought that just halting is quite bland. So, we designed it so that the text 'CG LEE' blinks on five of the 7-segment displays, during the halt state. We chose the text to express our respect and fondness for Professor Lee.



We needed a periodic clock signal to make the text blink. But the main clock is frozen, so we added a secondary clock 'haltCLK' which activates only at halt state. The code below shows the modified parts of `freqDivider.v` and `Proc.v`.

```

3  module freqDivider(
4      input clr,
5      input HALT,
6      input CLK,
7      output reg CLKout,
8      output reg haltCLKout
9  );
10
11  reg[31:0] cnt;
12  reg[31:0] haltCnt;
13
14  always @(posedge CLK) begin
15      if (clr) begin
16          cnt <= 32'd0;
17          haltCnt <= 32'd0;
18
19          CLKout <= 1'b1;
20          haltCLKout <= 1'b1;
21      end
22
23      else if(HALT == 0) begin // ordinary clock
24          if (cnt == 32'd0) begin // for simulation test
25              //if (cnt >= 32'd25000000) begin
26                  cnt <= 32'd0;
27                  CLKout <= ~CLKout;
28              end
29          else begin
30              cnt <= cnt + 1;
31          end
32      end
33      else begin // clock for events when HALT is given
34          if (haltCnt >= 32'd7500000) begin
35              haltCnt <= 32'd0;
36              haltCLKout <= ~haltCLKout;
37          end
38          else begin
39              haltCnt <= haltCnt + 1;
40          end
41      end
42  end
43 endmodule

```

```

53  assign segOut16 = (HALT == 0) ? sOut16 : ((haltCLK) ? 7'b1001110 : 0); // C
54  assign segOut1 = (HALT == 0) ? sOut1 : ((haltCLK) ? 7'b1011110 : 0); // G
55  assign segPc16 = (HALT == 0) ? sPc16 : ((haltCLK) ? 7'b0001110 : 0); // L
56  assign segPc1 = (HALT == 0) ? sPc1 : ((haltCLK) ? 7'b1001111 : 0); // E
57  assign segOpcode = (HALT == 0) ? op2seg : ((haltCLK) ? 7'b1001111 : 0); // E
58

```

Appendix. Test case programs used to test our design

Test program #1 (from final lab pdf)

Address	Machine code	Meaning		Expected Output
0x00	0100 1001	S2 <- Mem[S0+1]	S2 <- 1	0x01
0x01	1100 0001	PC <- (PC+1) + 1	Goto 0x03	0x00
0x02	0001 1000	S0 <- S1 + S2	(Skipped)	
0x03	1010 1001	Mem[S2+1] <- S2	Mem[2] <- 1	0x00
0x04	0100 1101	S3 <- S0 + 1	S3 <- 1	0x01
0x05	-	End		-

Expected output sequence:

(Start) -> 0x01 -> 0x00 -> 0xxx -> 0x01 -> (End)

Test program #2 (store and load test)

Address	Machine code	Meaning		Expected Output
0x00	0100 0001	S0 <- Mem[S0+1]	S0 <- 1	0x01
0x01	0000 0000	S0 <- S0 + S0	S0 <- 2	0x02
0x02	0000 0000	S0 <- S0 + S0	S0 <- 4	0x04
0x03	0100 0110	S1 <- Mem[S0-2]	S1 <- 2	0x02
0x04	0000 0110	S2 <- S0 + S1	S2 <- 6	0x06
0x05	1011 1001	Mem[S3+1] <- S2	Mem[1] <- 6	0x00
0x06	0111 1101	S3 <- Mem[S3+1]	S3 <- 6	0x06
0x07	0111 1111	S3 <- Mem[S3-1]	S3 <- 5	0x05
0x08	0010 1101	S1 <- S2 + S3	S1 <- 11	0x0b
0x09	0101 0001	S0 <- Mem[S1+1]	S0 <- 12	0x0c
0x0a	0000 1110	S2 <- S0 + S3	S2 <- 17	0x0b
0x0b	0110 0101	S1 <- Mem[S2+1]	S1 <- (-2)	0xfe
0x0c	-	End		-

Expected output sequence:

(Start) -> 0x01 -> 0x02 -> 0x04 -> 0x02 -> 0x06 -> 0x00 -> 0x06 -> 0x05 ->
 0x0b -> 0x0c -> 0x0b -> 0xfe -> (End)

Test program #3 (jump test)

Address	Machine code	Meaning		Expected Output
0x00	0100 0001	S0 <- Mem[S0+1]	S0 <- 1	0x01
0x01	1100 0001	PC <- (PC+1) + 1	Goto 0x03	0x00
0x02	1100 0001	PC <- (PC+1) + 1	(Skipped)	
0x03	0000 0000	S0 <- S0 + S0	S0 <- 2	0x02
0x04	1100 0001	PC <- (PC+1) + 1	Goto 0x06	0x00
0x05	1100 0001	PC <- (PC+1) + 1	(Skipped)	
0x06	0000 0000	S0 <- S0 + S0	S0 <- 4	0x04
0x07	1100 0001	PC <- (PC+1) + 1	Goto 0x09	0x00
0x08	1100 0001	PC <- (PC+1) + 1	(Skipped)	
0x09	0000 0000	S0 <- S0 + S0	S0 <- 8, 16, 32, ...	0x08, 0x10, 0x20, ...
0x0a	1100 0010	PC <- (PC+1) -2	Goto 0x09	0x00

Expected output sequence:

(Start) -> 0x01 -> 0x00 -> 0x02 -> 0x00 -> 0x04 -> 0x00 -> **0x08 -> 0x00 ->**
 0x10 -> 0x00 -> 0x20 -> 0x00 -> **0x00 -> ... (Infinite loop)**

Test program #4 (jump and load test)

Address	Machine code	Meaning		Expected Output
0x00	0100 0001	S0 <- Mem[S0+1]	S0 <- 1	0x01
0x01	1100 0001	PC <- (PC+1) + 1	Goto 0x03	0x00
0x02	1100 0001	PC <- (PC+1) + 1	(Skipped)	
0x03	0101 1001	S2 <- Mem[S1+1]	S2 <- 1	0x01
0x04	0010 1010	S2 <- S2 + S2	S2 <- 2	0x02
0x05	0010 1010	S2 <- S2 + S2	S2 <- 4	0x04
0x06	0010 1010	S2 <- S2 + S2	S2 <- 8	0x08
0x07	0010 1010	S2 <- S2 + S2	S2 <- 16	0x10
0x08	0010 1110	S2 <- S2 + S3	S2 <- 17	0x11
0x09	0110 1101	S3 <- Mem[S2+1]	S3 <- -1	0xff
0x0a	0000 1100	S0 <- S0 + S3	S0 <- S0 - 1	0x00, 0xff, 0xfe, ...
0x0b	1100 0010	PC <- (PC+1) - 2	Goto 0x0a	0x00

Expected output sequence:

(Start) -> 0x01 -> 0x00 -> 0x01 -> 0x02 -> 0x04 -> 0x08 -> 0x10 -> 0x11 ->
 0xff -> 0x00 -> **0x00 -> 0xff ->** **0x00 -> 0xfe -> 0x00 -> 0xfd ->**
 0x00 -> 0xfc -> ... (Infinite loop)